

Here are detailed, step-by-step instructions for building the dual transistor LED switch circuit from the schematic. I've included tips on how to identify the components from your salvaged parts.

Tools Needed

- Multimeter (essential for checking component values and continuity)
- Breadboard
- Jumper wires (solid core is best for breadboards)
- Wire strippers/cutters

Component Identification & Gathering

Before you begin building, let's find the parts from your collection.

1. NPN Transistors (Q1, Q2)

- **Schematic calls for:** 2N2222
- **From your parts:** Look for small, three-legged components with a black plastic case (usually TO-92 package).
 - **Read the number:** Look at the flat side of the transistor. Common general-purpose NPN transistors you might find include **2N2222, 2N3904, BC547, BC548, S8050**.
 - **Verify with a multimeter:** Set your multimeter to "diode test" mode.
 - Place the positive (red) probe on the center pin (usually the Base).
 - Touch the negative (black) probe to one of the other pins. You should get a reading between 0.6V and 0.7V.
 - Touch the black probe to the *other* outside pin. You should get a similar reading (0.6V - 0.7V).
 - If this works, the center pin is the **Base (B)**.
 - The pin with the slightly higher voltage reading is the **Emitter (E)**.
 - The pin with the slightly lower reading is the **Collector (C)**.
 - **Tip:** For the common 2N2222 in a TO-92 package, when looking at the flat face with pins pointing down, the pinout is usually **E-B-C** from left to right. Always

double-check with a datasheet if you're unsure.

2. Resistors (R1-R4)

You'll need to find two values. A multimeter set to resistance mode (Ω) is the most reliable way to check them.

- **10k Ω Resistors (R1, R3):**
 - **Color Codes:** Look for **Brown-Black-Orange** (followed by a tolerance band like Gold or Silver).
 - **Measurement:** Your multimeter should read close to 10,000 Ω (or 10 k Ω).
- **330 Ω Resistors (R2, R4):**
 - **Color Codes:** Look for **Orange-Orange-Brown**.
 - **Measurement:** Your multimeter should read close to 330 Ω . A value between 300 Ω and 470 Ω is acceptable for this circuit.

3. LEDs (D1, D2)

- **Identification:** Any standard red, green, or yellow LED will work.
- **Polarity is important!**
 - **Anode (+):** This is the longer leg. It connects towards the positive power supply. The outer plastic case is usually round on this side.
 - **Cathode (-):** This is the shorter leg. It connects towards the negative side (towards the transistor). The outer plastic case usually has a flat spot on this side.

4. Pushbuttons (S1, S2)

- **Identification:** Look for momentary tactile switches. They usually have four small legs.
- **Testing:** Use your multimeter in continuity mode (it should beep when probes touch).
 - Place probes on two legs on opposite sides of the switch body.
 - Press the button. The multimeter should beep, indicating a connection is made.
 - Release the button. The beeping should stop.
 - Find two pairs of legs that work this way. For the circuit, you'll use one of these pairs for each button.

5. Power Source (BT1)

- A fresh **9V battery** and a snap connector with red (+) and black (-) wires.
-

Step-by-Step Assembly Instructions

We will build the circuit on a breadboard. We'll establish the power rails first, then build Circuit 1 (left side of schematic), and then Circuit 2 (right side).

Step 1: Set up Power Rails

1. Take your breadboard. The long red and blue/black lines on the edges are for power distribution.
2. Connect the **red wire** from your 9V battery snap to the **red (+)** rail on the breadboard.
3. Connect the **black wire** from your 9V battery snap to the **blue/black (-)** rail. This is your Ground (GND).

Step 2: Build Circuit 1 (Q1, D1, S1)

1. **Place the Transistor (Q1):** Insert your NPN transistor into the breadboard such that each of its three legs is in a separate row (e.g., rows 10, 11, 12). Note which leg is Emitter, Base, and Collector.
2. **Connect Emitter to Ground:** Use a jumper wire to connect the **Emitter (E)** leg of Q1 directly to the **negative (-) power rail**.
3. **Place the Pushbutton (S1):** Insert the pushbutton across the center channel of the breadboard so its legs are separated.
4. **Connect Power to Button:** Connect one leg of the pushbutton to the **positive (+) power rail**.
5. **Connect Button to Base:**
 - Insert one end of the **10kΩ resistor (R1)** into the same row as the *other* leg of the pushbutton.

- Insert the other end of **R1** into the same row as the **Base (B)** leg of the transistor (Q1).

6. Place the LED and its Resistor:

- Insert one end of the **330Ω resistor (R2)** into the **positive (+) power rail**.
- Insert the other end into an unused row on the breadboard.
- Insert the **Anode (longer leg)** of the **LED (D1)** into the *same row* as the resistor you just placed.
- Insert the **Cathode (shorter leg, flat side)** of the LED into the same row as the **Collector (C)** leg of the transistor (Q1).

Test Circuit 1: Snap the 9V battery onto the connector. Press button S1. LED D1 should light up. If not, disconnect the battery and double-check all connections, especially the orientation of the LED and transistor.

Step 3: Build Circuit 2 (Q2, D2, S2)

This is an exact copy of the first circuit, built on another part of the breadboard.

- 1. Place Transistor (Q2):** Insert the second NPN transistor into new rows.
- 2. Connect Emitter to Ground:** Connect the **Emitter (E)** of Q2 to the **negative (-) power rail**.
- 3. Place Pushbutton (S2):** Insert the second button.
- 4. Connect Power to Button:** Connect one leg of S2 to the **positive (+) power rail**.
- 5. Connect Button to Base:** Connect the second **10kΩ resistor (R3)** from the other leg of S2 to the **Base (B)** of Q2.
- 6. Place LED and Resistor:**
 - Connect the second **330Ω resistor (R4)** from the **positive (+) power rail** to a new row.
 - Connect the **Anode** of the second **LED (D2)** to that same row.
 - Connect the **Cathode** of D2 to the **Collector (C)** of Q2.

Final Test

Reconnect the 9V battery.

- Press **S1**: LED **D1** should turn on.
- Press **S2**: LED **D2** should turn on.
- Press both: Both LEDs should turn on independently.

You have successfully built the dual transistor switching circuit from the schematic!